

ECE 483: Analog IC Design
Final Report
Low Dropout Regulator

Sayankar, Rutvik
rutviks2@illinois.edu

Patel, Dev
dpatel2@illinois.edu

May 3, 2024

1. Overall Design Approach

1.1 Design choices

asdf

1.2 System level trade-offs

asdf

2. Schematic & Parameters

2.1 Schematic

2.2 Device Parameters


Device	W(μm)	L(nm)	Multiplier	$g_m(\mu\text{S})$	$r_{ds}(\text{ohms})$	Vov(mV)	$I_{bias}(\mu\text{A})$
MPass	1.08	270	500	12.41m	5.864k	106.1	800
MP0	1.44	270	24	881.1	23.07k	114.7	60
MP1	1.44	270	24	911.2	770.3k	108.5	59.99
MP2	1.44	270	24	552.5	161.7k	57.96	29.96
Mp3	1.44	270	24	552	161.9k	58.41	29.97
MP4	1.44	270	4	148.7	132.3k	116.1	10.2
MP5	1.44	270	4	154	466.9k	109.5	10.2
MP6	1.44	270	4	148.7	131.9k	116.1	10.19
MP7	1.44	270	4	153.9	459.8k	109.6	10.19
MP8	1.44	270	4	147.6	148.5k	114.7	10.03
MP9	1.44	270	4	153	562.2k	104.2	10.03
MP10	1.44	270	4	147	139k	114.7	10
MP11	1.44	270	4	152	473.1k	108.2	10
MN0	.72	540	6	174.5	596.1k	89.27	10.2
MN2	.72	540	8	444	69.14k	177.1	40.17
MN4	.72	540	6	172	511.6k	90.43	10.03
MN5	.72	540	2	110.7	263.9k	177.1	10.03
MN6	.72	540	6	174.5	596.7k	89.22	10.19
MN7	.72	540	8	444.1	69.22k	177.1	40.17

3. Performance


3.1 Simulation Results

Design Parameter/Variable	Specification	Simulated Performance
Input Voltage	$1.8V \pm 10\%$	1.8V
Output Voltage	1.0V - 1.4V	1.0V - 1.4V
Load Current	0.1mA - 10mA	0.1mA - 10mA
DC Load Regulation	$\leq 50\mu V/mA$	$15.55\mu V/mA$
DC Line Regulation	$\leq 500\mu V/V$	$750\mu V/V$
Quiescent Current	Minimum	$600\mu A$
PSR (@Fin = 1KHz/Fin = 1MHz)	-	-72.97dB/-12.31dB
Worst-case PSR	-	-1.42dB
DC loop gain (IL=0.1mA/IL=10mA)	-	86.22 dB / 75.64 dB
Loop-gain unity-gain frequency (IL=0.1mA/IL=10mA)	-	3.981 MHz / 3.479 MHz
Loop-gain phase margin(IL=0.1mA/IL=10mA)	-	62.4° / 82.35°
Loop-gain gain margin (IL=0.1mA/IL=10mA)	-	23.61 dB / 28.72 dB
Output noise (IL=0.1mA/IL=10mA)	-	$61.3\mu V$ / $58.1\mu V$

3.1.1 Loop-gain AC response

 

 3.1.2 DC load and line regulation response



3.1.3 Power supply rejection (PSR)

 


Figure 3.1: PSR with Minimum Load Current

 


Figure 3.2: PSR with Maximum Load Current